

**DIPLOMA EXAMINATION IN ENGINEERING/TECHNOLOGY/
MANAGEMENT/COMMERCIAL PRACTICE, NOVEMBER – 2023**

LINEAR INTEGRATED CIRCUITS

[Maximum Marks: **100**]

[Time: **3 Hours**]

PART-A

[Maximum Marks: **10**]

I. (Answer *all* questions in one or two sentences. Each question carries **2** marks)

1. Define Slew rate.
2. What is input offset voltage?
3. List the applications of integrator.
4. Define lock range of a PLL.
5. State the principle of opto-couplers.

(5 x 2 = 10)

PART-B

[Maximum Marks: **30**]

II. (Answer *any five* of the following questions. Each question carries **6** marks)

1. List the different parameters of op amp.
2. Describe the working of a first order Butterworth LPF.
3. Write short notes on integrator.
4. Explain the working of LM 380 audio power amplifier.
5. Explain the general block diagram of a PLL.
6. Draw the block diagram of dual power supply.
7. List the advantages and disadvantages of SMPS.

(5 x 6 = 30)

PART-C

[Maximum Marks: **60**]

(Answer *one* full question from each Unit. Each full question carries **15** marks)

UNIT – I

- III. a. Draw the block diagram of an op-amp and explain each block. (8)
- b. Explain the working of a voltage follower circuit using op-amp. (7)

OR

- IV. a. Explain the different op-amp packages. (8)
- b. With circuit diagram explain the working of an inverting amplifier. (7)

UNIT – II

- V. a. Explain the working of a full wave precision rectifier. (8)
- b. Describe the working of a Schmitt trigger circuit using op-amp. (7)

OR

- VI. a. Briefly explain the principle of an RC phase shift oscillator using op-amp. (8)
- b. Explain the working of Triangular wave generator. (7)

UNIT- III

- VII. a. Draw the internal architecture of 555 timer and explain. (9)
- b. Explain the block diagram of frequency multiplier using PLL. (6)

OR

- VIII. a. Explain the block diagram of VCO 566. (8)
- b. Explain the block diagram of FM demodulator using PLL. (7)

UNIT - IV

- IX. a. Explain the basic block diagram of an SMPS. (8)
- b. Explain the fixed positive voltage regulators. (7)

OR

- X. a. Explain the functional block diagram of LM 723 voltage regulator. (8)
- b. With circuit diagram explain the operation of adjustable voltage regulator using LM 317. (7)
